

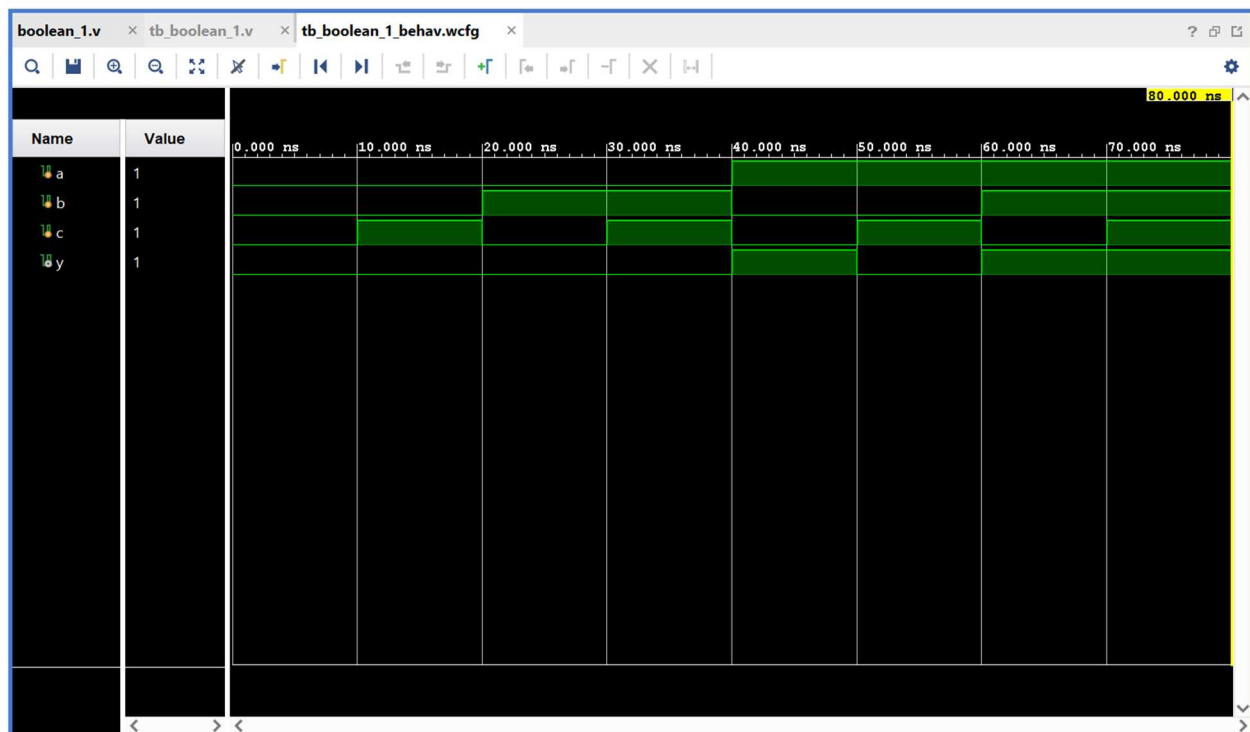
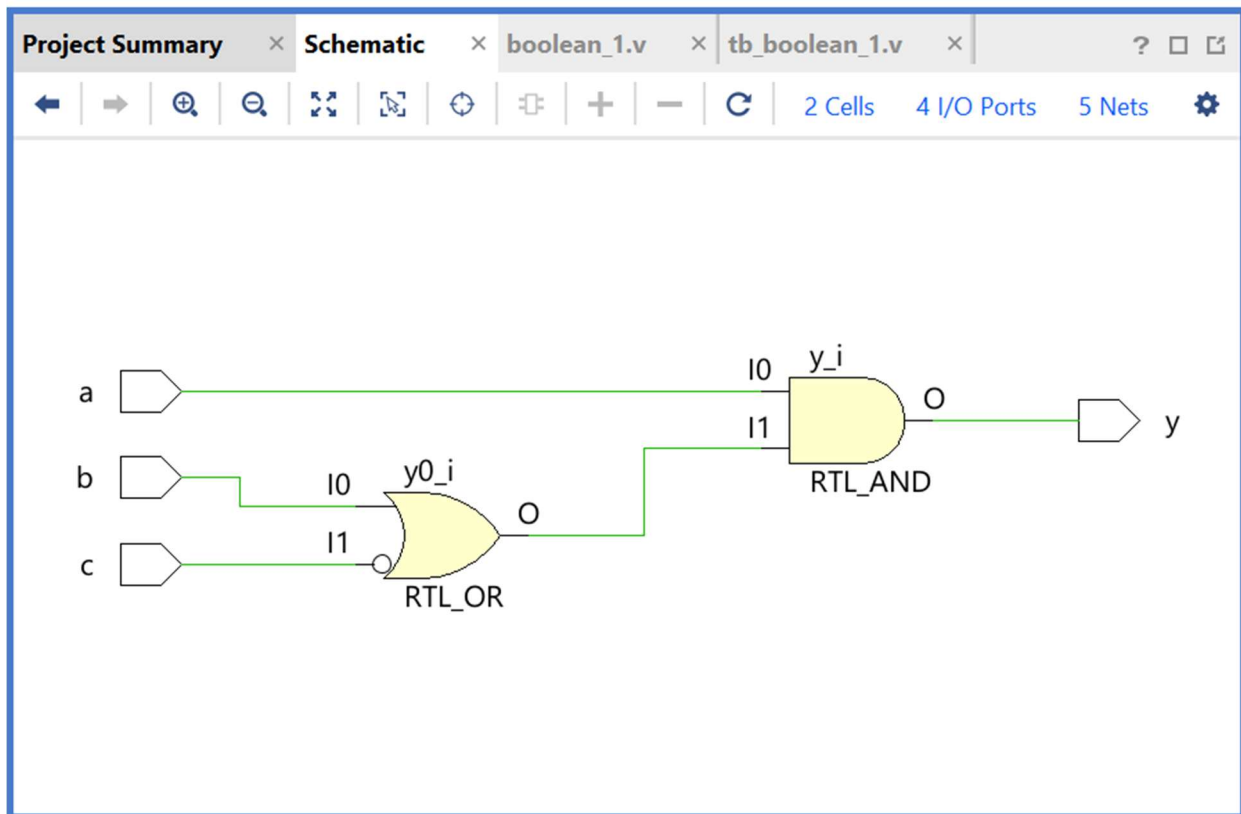




BOOLEAN 1: $Y = A.(B+(\sim C))$

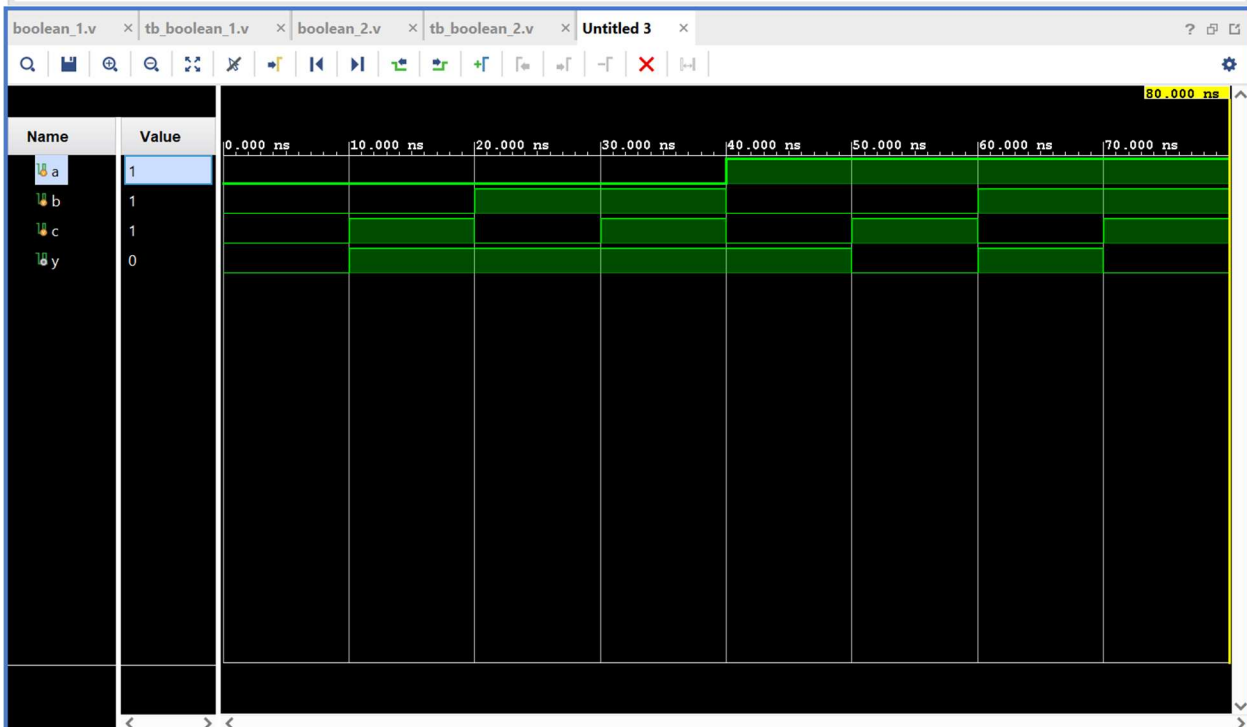

BOOLEAN 2: $Y=((\sim A).(B+C)) + ((A+B).(\sim C))$

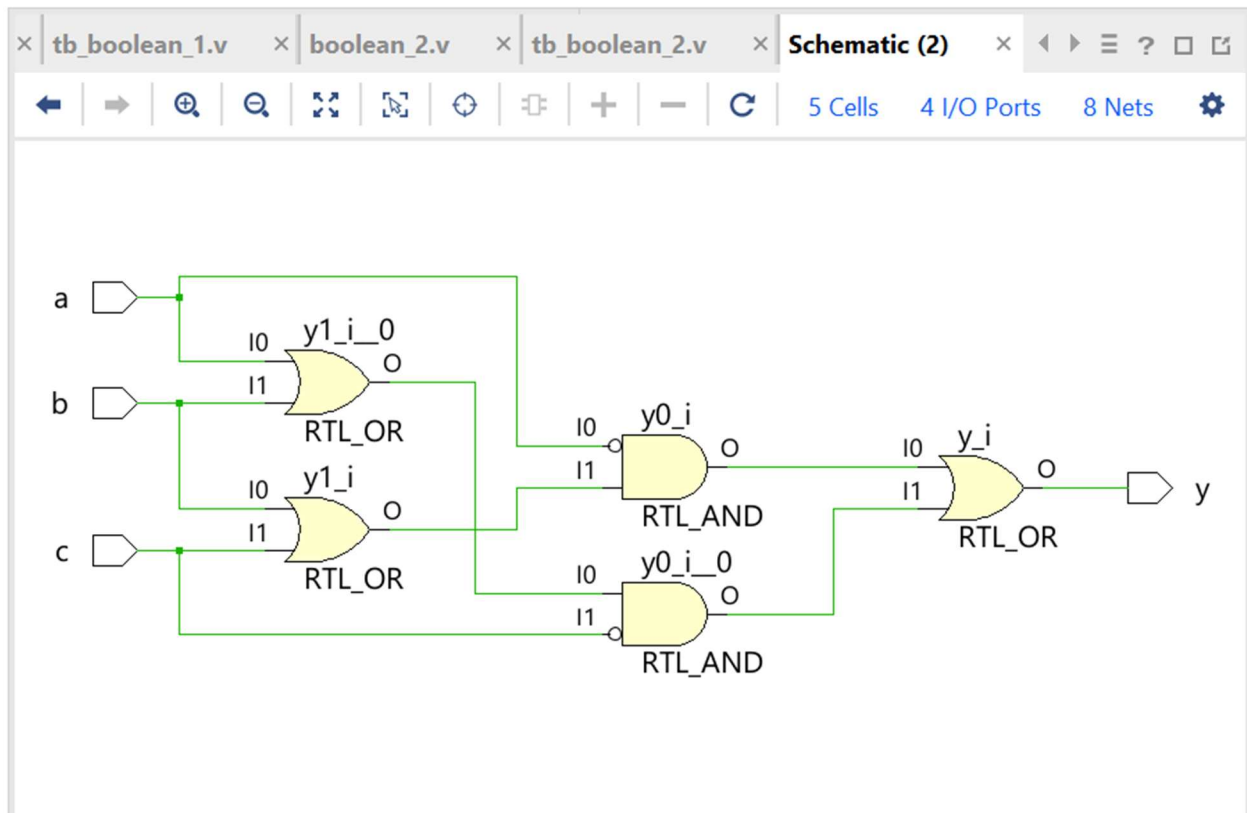

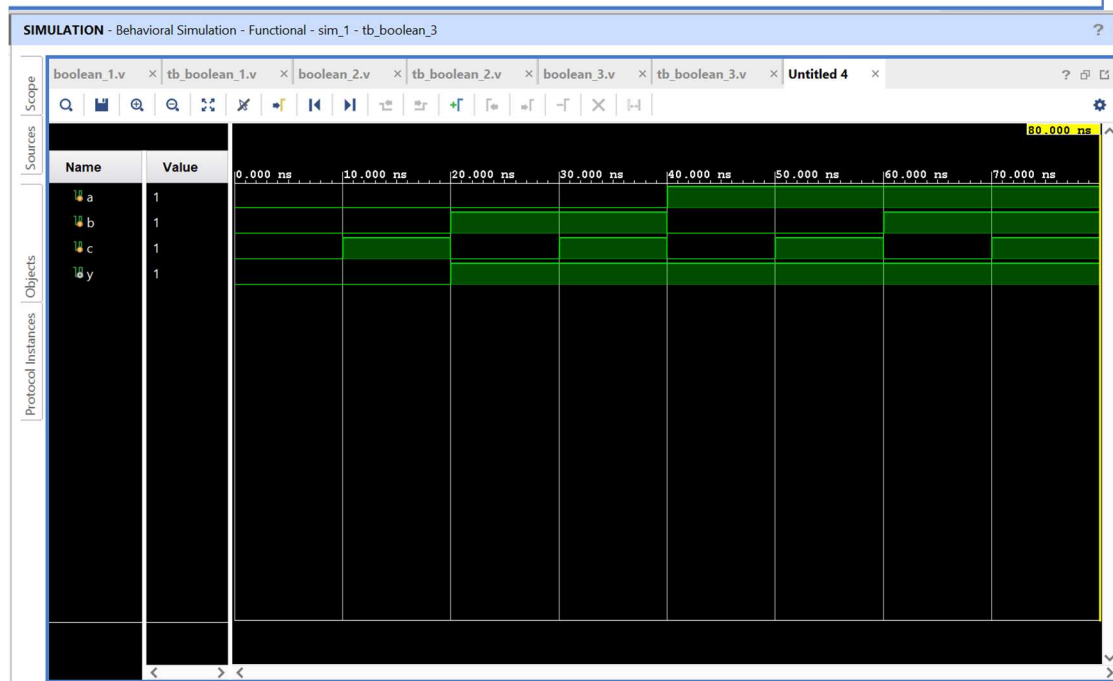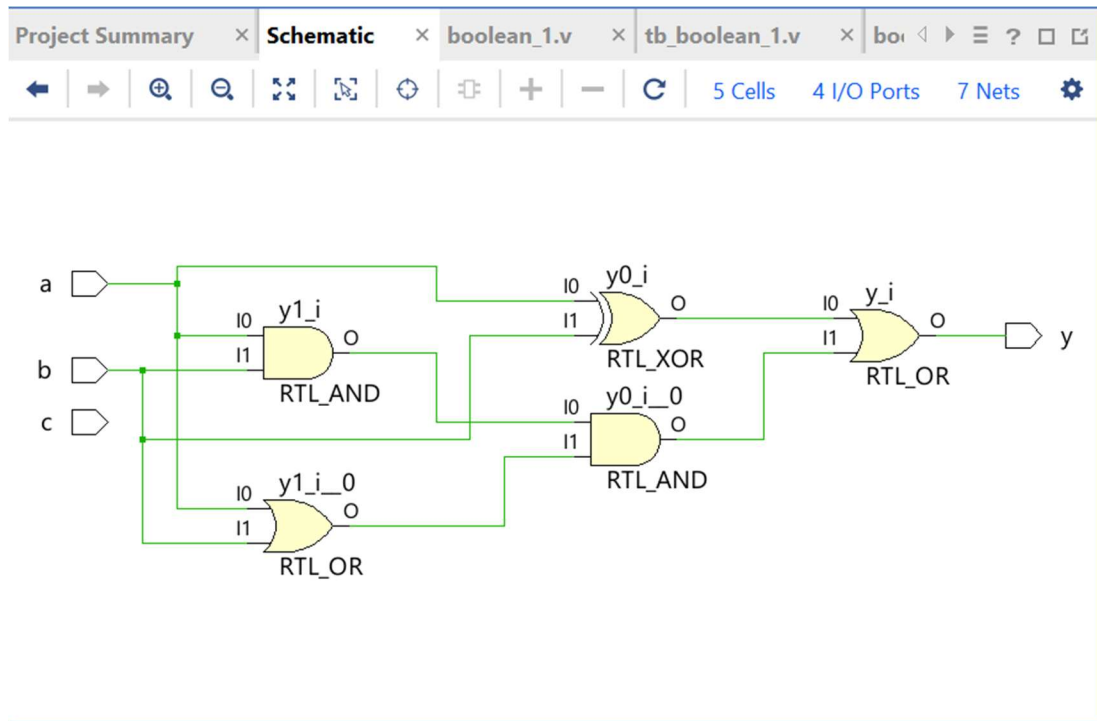BOOLEAN 3: $Y = (A \text{ XOR } B) + ((A.B).(A+B))$



If you see the simulation, 'c' is treated as don't care condition because actual Boolean expression uses 'a' & 'b' as input but in code, I take 'a', 'b' and 'c' as inputs to show that it will not affect the circuit diagram and simulation. But treated 'c' as don't care.